
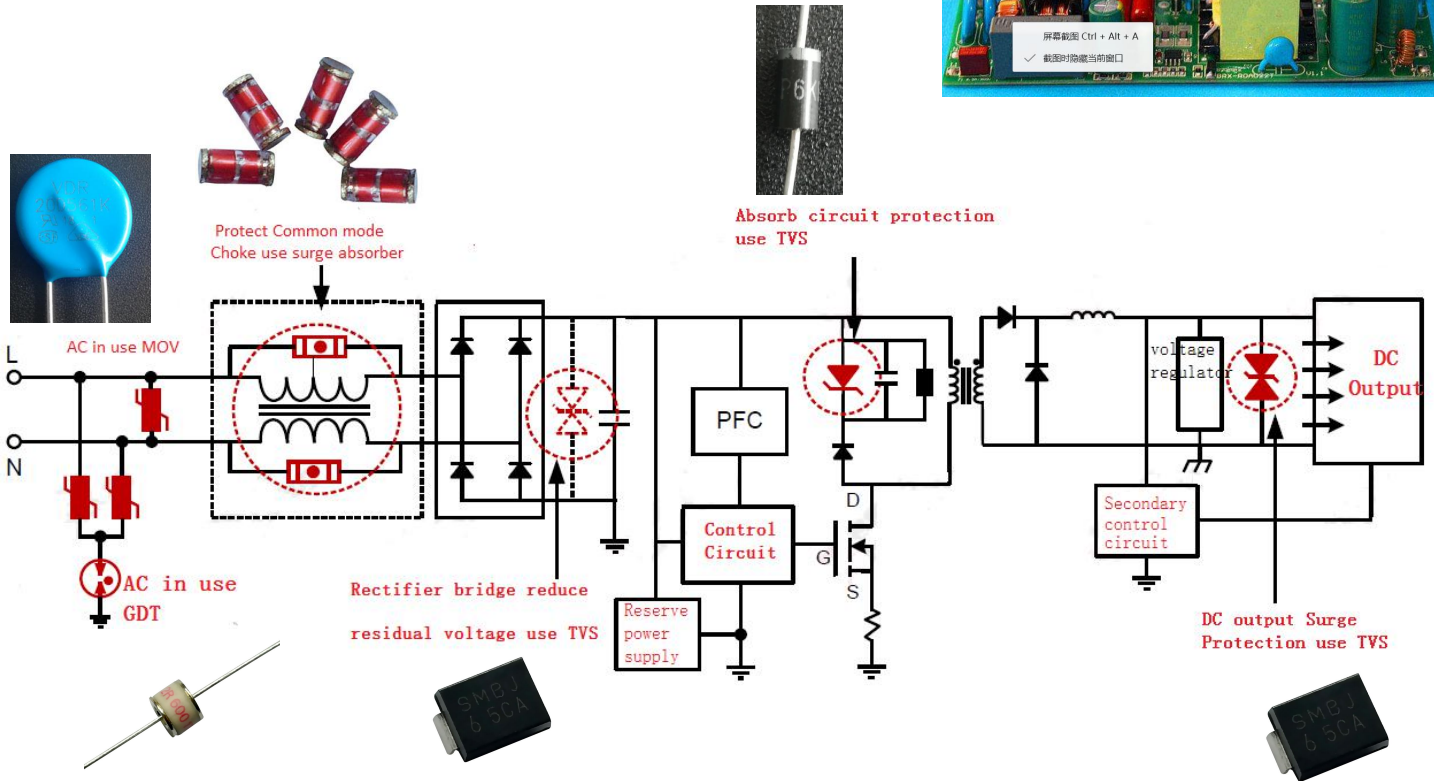


▼ AC220V Solution:

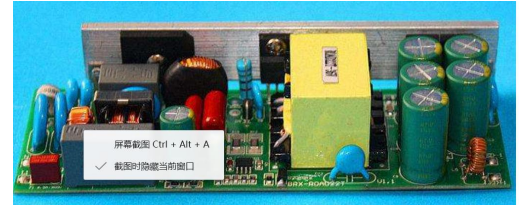Surge level: 1.2/50us-8/20us CM/DM 10KV-5KA



Circuit Protection Components Usage	
AC in use MOV	VDR-20D561K *3
AC in use GDT	HA2R8-600ML *1
Protect Common mode Choke use surge absorber	JSE-301M-2667 / JSE-301M-SMB *2
Rectifier bridge reduce residual voltage use TVS	P6KE440CA / SMBJ400CA* 1
Absorb circuit protection use TVS	P6KE200A / P6KE200CA* 1
DC output Surge Protection use TVS	DC3.3V: SMAJ5.0A/SMBJ5.0A /SMCJ5.0A DC5V: SMAJ6.5A /SMBJ6.5A /SMCJ6.5A DC12V: SMAJ18A /SMBJ18A /SMCJ18A DC24V: SMAJ28A /SMBJ28A /SMCJ28A

We focus on development, production,distribution of GDT,TSS.MOV,TVS,ESD,PTC component.We have laboratories of EMC,aiming to provide total turnkey service of surge/ESD test and circuit PCB improvement.

sales@huaandz.com